

Laboratory Exercise 7

Finite State Machines

This is an exercise in using finite state machines.

Part I

We wish to implement a finite state machine (FSM) that recognizes two specific sequences of applied input symbols, namely four consecutive 1s or four consecutive 0s. There is an input w and an output z . Whenever $w = 1$ or $w = 0$ for four consecutive clock pulses the value of z has to be 1; otherwise, $z = 0$. Overlapping sequences are allowed, so that if $w = 1$ for five consecutive clock pulses the output z will be equal to 1 after the fourth and fifth pulses. Figure 1 illustrates the required relationship between w and z .

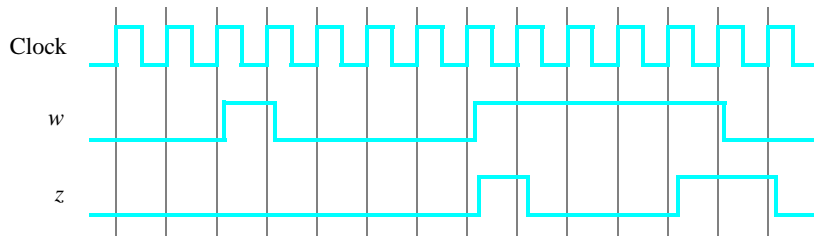


Figure 1: Required timing for the output z .

A state diagram for this FSM is shown in Figure 2. For this part you are to manually derive an FSM circuit that implements this state diagram, including the logic expressions that feed each of the state flip-flops. To implement the FSM use nine state flip-flops called y_8, \dots, y_0 and the one-hot state assignment given in Table 1.

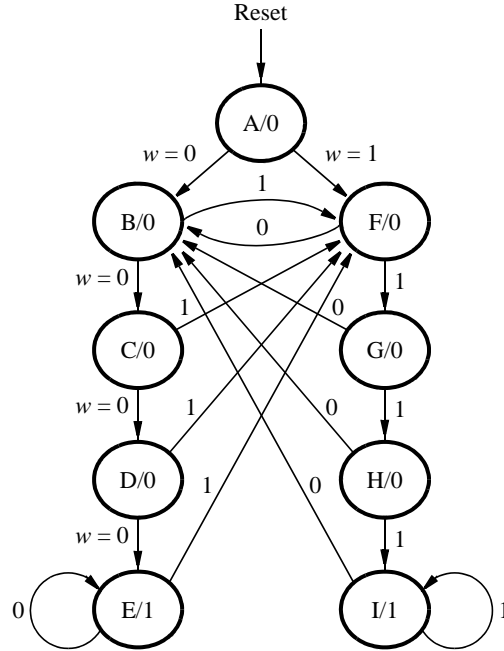


Figure 2: A state diagram for the FSM.

Name	State Code
	$y_8y_7y_6y_5y_4y_3y_2y_1y_0$
A	000000001
B	000000010
C	000000100
D	000001000
E	000010000
F	000100000
G	001000000
H	010000000
I	100000000

Table 1: One-hot codes for the FSM.

Design and implement your circuit on your DE-series board as follows:

1. Create a new Quartus II project for the FSM circuit.
2. Write a VHDL file that instantiates the nine flip-flops in the circuit and which specifies the logic expressions that drive the flip-flop input ports. Use only simple assignment statements in your VHDL code to specify the logic feeding the flip-flops. Note that the one-hot code enables you to derive these expressions by inspection.
Use the toggle switch SW_0 as an active-low synchronous reset input for the FSM, use SW_1 as the w input, and the pushbutton KEY_0 as the clock input which is applied manually. Use the red light $LEDR_9$ as the output z , and assign the state flip-flop outputs to the red lights $LEDR_8$ to $LEDR_0$.
3. Include the VHDL file in your project, and assign the pins on the FPGA to connect to the switches and the LEDs.

4. Simulate the behavior of your circuit.
5. Once you are confident that the circuit works properly as a result of your simulation, download the circuit into the FPGA chip. Test the functionality of your design by applying the input sequences and observing the output LEDs. Make sure that the FSM properly transitions between states as displayed on the red LEDs, and that it produces the correct output values on $LEDR_9$.
6. Finally, consider a modification of the one-hot code given in Table 1. It is often desirable to set all flip-flop outputs to the value 0 in the reset state.

Table 2 shows a modified one-hot state assignment in which the reset state, A, uses all 0s. This is accomplished by inverting the state variable y_0 . Create a modified version of your VHDL code that implements this state assignment. (*Hint*: you should need to make very few changes to the logic expressions in your circuit to implement the modified state assignment.)

7. Compile your new circuit and test it.

Name	State Code
	$y_8y_7y_6y_5y_4y_3y_2y_1y_0$
A	000000000
B	000000011
C	000000101
D	000001001
E	000010001
F	000100001
G	001000001
H	010000001
I	100000001

Table 2: Modified one-hot codes for the FSM.

Part II

For this part you are to write another style of Verilog code for the FSM in Figure 2. In this version of the code you should not manually derive the logic expressions needed for each state flip-flop. Instead, describe the state table for the FSM by using a VHDL CASE statement in a PROCESS block, and use another PROCESS block to instantiate the state flip-flops. You can use a third PROCESS block or simple assignment statements to specify the output z . To implement the FSM, use four state flip-flops y_3, \dots, y_0 and binary codes, as shown in Table 3.

Name	State Code
	$y_3y_2y_1y_0$
A	0000
B	0001
C	0010
D	0011
E	0100
F	0101
G	0110
H	0111
I	1000

Table 3: Binary codes for the FSM.

A suggested skeleton of the VHDL code is given in Figure 3.

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY part2 IS
    PORT ( ... define input and output ports
          ...);
END part2;

ARCHITECTURE Behavior OF part2 IS
    ... declare signals
    TYPE State_type IS (A, B, C, D, E, F, G, H, I);
    -- Attribute to declare a specific encoding for the states
    attribute syn_encoding : string;
    attribute syn_encoding of State_type : type is "0000 0001 0010 0011 0100 0101 0110 0111 1000";

    SIGNAL y_Q, Y_D : State_type; -- y_Q is present state, y_D is next state
BEGIN
    ...
    PROCESS (w, y_Q) -- state table
    BEGIN
        case y_Q IS
            WHEN A IF (w = '0') THEN Y_D <= B;
                    ELSE Y_D <= F;
                    END IF;
            ... other states
        END CASE;
    END PROCESS; -- state table

    PROCESS (Clock) -- state flip-flops
    BEGIN
        ...
    END PROCESS;

    ... assignments for output z and the LEDs
END Behavior;
```

Figure 3: Skeleton VHDL code for the FSM.

Implement your circuit as follows.

1. Create a new project for the FSM.
2. Include in the project your VHDL file that uses the style of code in Figure 3. Use the same switches, pushbuttons, and lights that were used in Part I.
3. Before compiling your code it is necessary to explicitly tell the Synthesis tool in Quartus II that you wish to have the finite state machine implemented using the state assignment specified in your VHDL code. If you do not explicitly give this setting to Quartus II, the Synthesis tool will automatically use a state assignment of its own choosing, and it will ignore the state codes specified in your VHDL code. To make this setting, choose **Assignments > Settings** in Quartus II, and click on the **Analysis and Synthesis** item on the left

side of the window, then click on the **More Setting** button. As indicated in Figure 4, change the parameter **State Machine Processing** to the setting **User-Encoded**.

4. Compile your project. To examine the circuit produced by Quartus II open the RTL Viewer tool. Double-click on the box shown in the circuit that represents the finite state machine, and determine whether the state diagram that it shows properly corresponds to the one in Figure 2. To see the state codes used for your FSM, open the Compilation Report, select the **Analysis and Synthesis** section of the report, and click on **State Machines**.
5. Download the circuit into the FPGA chip and test its functionality.
6. In step 3 you instructed the Quartus II Synthesis tool to use the state assignment given in your VHDL code. To see the result of removing this setting, open again the Quartus II settings window by choosing **Assignments > Settings**, and click on the **Analysis and Synthesis** item, then click on the **More Setting** button. Change the setting for **State Machine Processing** from **User-Encoded** to **One-Hot**. Recompile the circuit and then open the report file, select the **Analysis and Synthesis** section of the report, and click on **State Machines**. Compare the state codes shown to those given in Table 2, and discuss any differences that you observe.

 


Figure 4: Specifying the state assignment method in Quartus II.

Part III

The sequence detector can be implemented in a straightforward manner using shift registers, instead of using the more formal approach described above. Create VHDL code that instantiates two 4-bit shift registers; one is for recognizing a sequence of four 0s, and the other for four 1s. Include the appropriate logic expressions in your design to produce the output z . Make a Quartus II project for your design and implement the circuit on your DE-series board. Use the switches and LEDs on the board in a similar way as you did for Parts I and II and observe the behavior of your shift registers and the output z . Answer the following question: could you use just one 4-bit shift register, rather than two? Explain your answer.

Part IV

In this part of the exercise you are to implement a Morse-code encoder using an FSM. The Morse code uses patterns of short and long pulses to represent a message. Each letter is represented as a sequence of dots (a short pulse), and dashes (a long pulse). For example, the first eight letters of the alphabet have the following representation:

A	• —
B	— • • •
C	— • — •
D	— • •
E	•
F	• • — •
G	— — •
H	• • • •

Design and implement a Morse-code encoder circuit using an FSM. Your circuit should take as input one of the first eight letters of the alphabet and display the Morse code for it on a red LED. Use switches SW_{2-0} and pushbuttons KEY_{1-0} as inputs. When a user presses KEY_1 , the circuit should display the Morse code for a letter specified by SW_{2-0} (000 for A, 001 for B, etc.), using 0.5-second pulses to represent dots, and 1.5-second pulses to represent dashes. Pushbutton KEY_0 should function as an asynchronous reset.

A high-level schematic diagram of a possible circuit for the Morse-code encoder is shown in Figure 5.

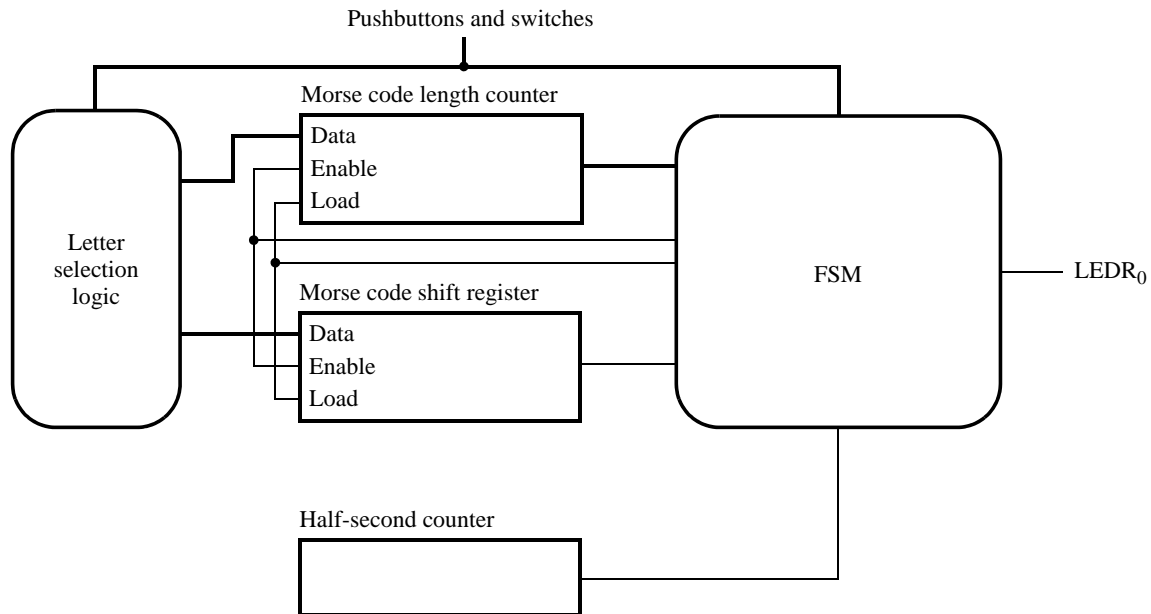


Figure 5: High-level schematic diagram of the circuit for Part IV.